

Name: Sifat Abdullah

ID: 19101384

Sec: 01

CSE350 (lab 0)

Report

OR

OR Gate:

| V_A | V_B | V_{R1} | V_{R2} | I_{R1} | I_{R2} | $V_R = Y$ |
|-------|-------|----------|----------|----------------------|----------------------|-----------|
| 5 | 5 | 0 | 0 | 2.2×10^{-5} | 2.2×10^{-5} | 4.4349 |
| 5 | 0 | 0.01 | 0 | 4.4×10^{-5} | 4.4×10^{-5} | 4.4087 |
| | | | | | | |
| | | | | | | |

① ans: in diode AND circuit we can see when one ~~output~~^{input} is high and other input is low then the output is low, but when both the input is low the output is also low ~~but~~ when both the circuit is high the output is also high which is what we expect from an AND gate.

2) If we change the value of $V_A = V_B = 6$ in the software the output is still same as 5V. so the diode is working.

OR Gate:

| Va | Vb | Vr1 | Vr2 | Ir1 | Ir2 | Vr=Y |
|----|----|-----|-----|-----------|-----------|-----------|
| 5 | 5 | 0 | 0 | 2.21e-005 | 2.21e-005 | 4.4349 |
| 5 | 0 | 0.1 | 0 | 4.4e-005 | 4.4e-012 | 4.4087 |
| 0 | 5 | 0 | 0.1 | 4.4e-012 | 4.4e-005 | 4.4087 |
| 0 | 0 | 0 | 0 | 1.19e-02 | 1.19e-02 | 1.38e-015 |

And Gate:

| Va | Vb | Vr1 | Vr2 | Ir1 | Ir2 | Vr=Y |
|----|----|-------|-------|-----------|-----------|--------|
| 5 | 5 | 0 | 0 | 5e-012 | 5e-012 | 5 |
| 5 | 0 | 0 | -0.01 | 9.41e-012 | 4.4e-005 | 0.591 |
| 0 | 5 | -0.01 | 0 | 4.4e-005 | 9.41e-012 | 0.591 |
| 0 | 0 | 0 | 0 | 2.21e-005 | 2.21e-005 | 0.5651 |

Inverter:

| vi | Vr1 | Vr2 | vrc | I1 | I2 | ib | ic | Y |
|----|------|------|-------|-----------|----------|------------|----------|-------|
| 5 | 4.3 | 5.7 | -4.89 | 0.0002 | 5.7e-005 | 0.0002 | 0.002 | 0.108 |
| 0 | 0.65 | 4.35 | 0 | 4.35e-005 | 4.3e-005 | 3.196e-012 | 1.7e-011 | 5 |



